

# University of Mauritius

Faculty of Information ,Communication and Digital  
Technologies

## Computer Architecture and Organisation Assignment 1

Prepared by :

SOOBRAYEN Keshia 2412920

BEEDASSY Nirvana Luxmi 2413850

RAGHOONUNDUN Rishab 2412024

AUCKEL Ayush Manav 2412549

THUMMANAH Kentish 2411831

Course : BSc (Hons) Computer Science Level 1

Module : ICT 1206Y Computer Architecture and Organisation

## Table of Contents

1. Sequence recognition problem.....	1
1.1 State transition diagram .....	1
1.2 State table.....	2
1.3 Assigned binary code to states .....	2
1.4 Determined flip-flop input values .....	2
1.5 Karnaugh maps .....	3
1.6 Logic circuits.....	4
1.6.1 Subcircuits.....	4
1.6.2 Main circuit .....	5
1.7 Circuit simulation.....	5
2. Vending machine problem .....	12
2.1 State transition diagram .....	12
2.2 State table.....	13
2.3 Assigned binary code to states .....	13
2.4 Determined flip-flop input values .....	14
2.5 Karnaugh maps .....	15
2.6 Logic circuits .....	16
2.6.1 Subcircuits.....	16
2.6.2 Main circuit.....	17
2.7 Circuit simulation.....	17

# 1. Sequence recognition problem

Implement a circuit (one input X and one output Z) that recognizes the occurrence of the sequence of bits 1001 on the input X by making the output Z equal to 1 when the previous three inputs to the circuit were 100 and current input is a 1. Use D flip-flops.


For example:

X: 0 0 1 1 0 0 1 0 0 1 1 0 1 0 0 1 1 1 . . . .

Z: 0 0 0 0 0 0 1 0 0 1 0 0 0 0 0 1 0 0 . . . .

## 1.1 State transition diagram

State	Meaning	$Q_1 Q_0$
A	No valid sequence detected	0 0
B	Sequence 1 detected	0 1
C	Sequence 10 detected	1 0
D	Sequence 100 detected	1 1

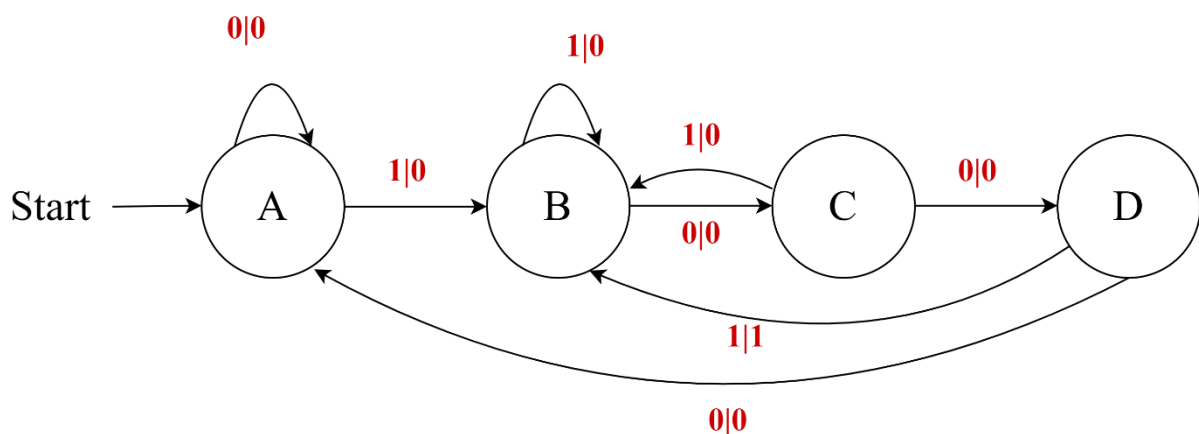

Notation : X|Z

## 1.2 State table

Present State	Input	Next State	Output
A	0	A	0
A	1	B	0
B	0	C	0
B	1	B	0
C	0	D	0
C	1	B	0
D	0	A	0
D	1	B	1

State	Q <sub>1</sub> Q <sub>0</sub>
A =	0 0
B =	0 1
C =	1 0
D =	1 1

## 1.3 Assigned binary code to states

Present State		Input	Next State		Output
Q <sub>1</sub>	Q <sub>0</sub>	X	Q <sub>1</sub>	Q <sub>0</sub>	Z
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	1	1	0
1	0	1	0	1	0
1	1	0	0	0	0
1	1	1	0	1	1

## 1.4 Determined flip-flop input values

Present State		Input	Next State		Flip-Flop		Output
Q <sub>1</sub>	Q <sub>0</sub>	X	Q <sub>1</sub>	Q <sub>0</sub>	D <sub>1</sub>	D <sub>0</sub>	Z
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	1	0	1	0	0
0	1	1	0	1	0	1	0
1	0	0	1	1	1	1	0
1	0	1	0	1	0	1	0
1	1	0	0	0	0	0	0
1	1	1	0	1	0	1	1

**D excitation table :**

$Q_1$	$Q_0$	$D$	Operation
0	0	0	Reset
0	1	1	Set
1	0	0	Reset
1	1	1	Set

## 1.5 Karnaugh maps

For  $D_1$  :

		$Q_0X$			
		00	01	11	10
$Q_1$	0	0	0	0	1
	1	1	0	0	0

$$D_1 = \bar{Q}_1 Q_0 \bar{X} + Q_1 \bar{Q}_0 \bar{X}$$

For  $D_0$  :

		$Q_0X$			
		00	01	11	10
$Q_1$	0	0	1	1	0
	1	1	1	1	0

$$D_0 = X + Q_1 \bar{Q}_0$$




For  $Z$  :

		$Q_0X$			
		00	01	11	10
$Q_1$	0	0	0	0	0
	1	0	0	1	0

$$Z = Q_1 Q_0 X$$


## 1.6 Logic circuits

### 1.6.1 Subcircuits

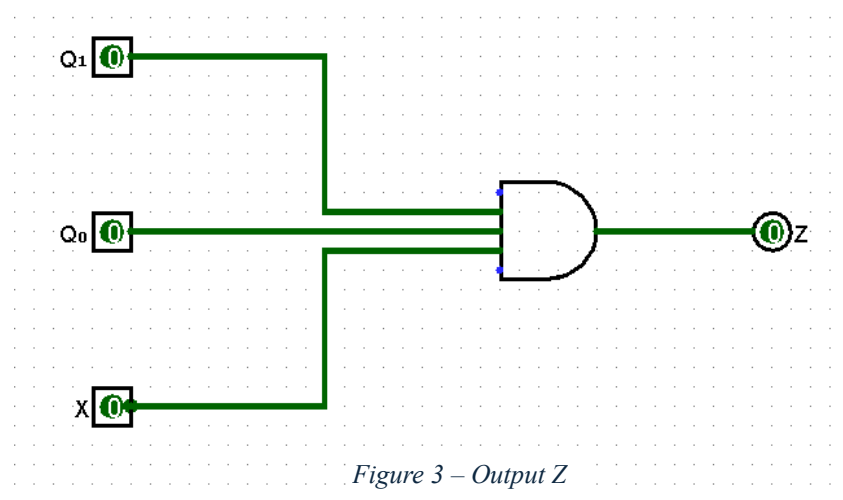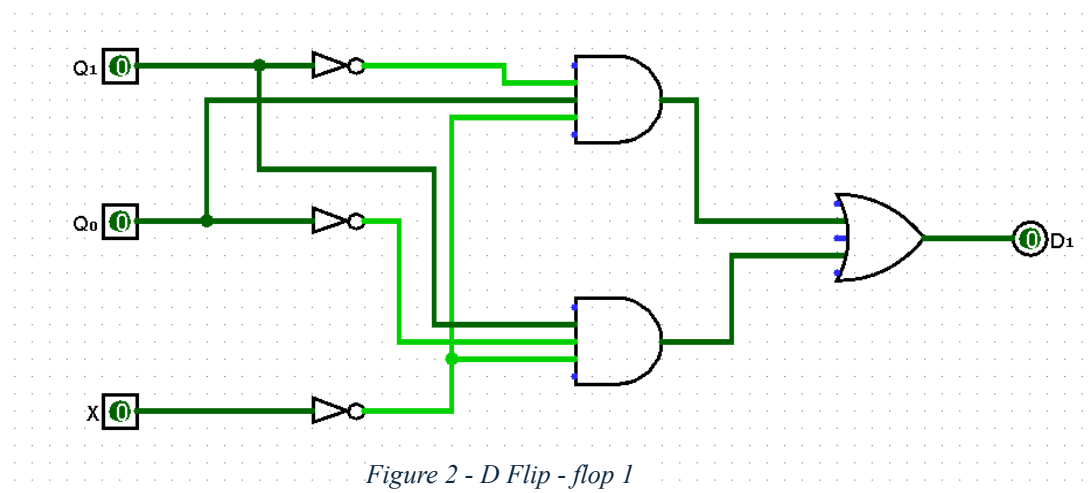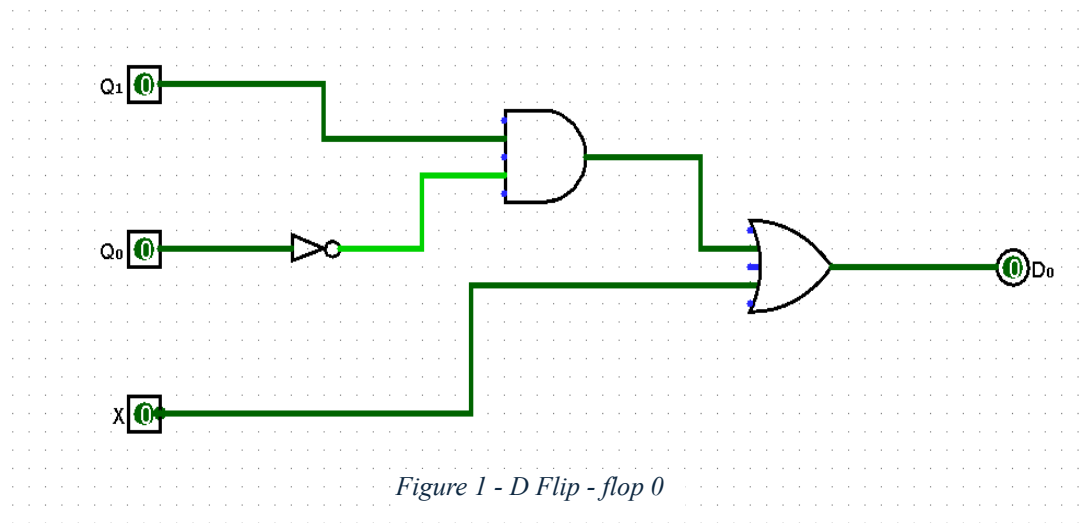
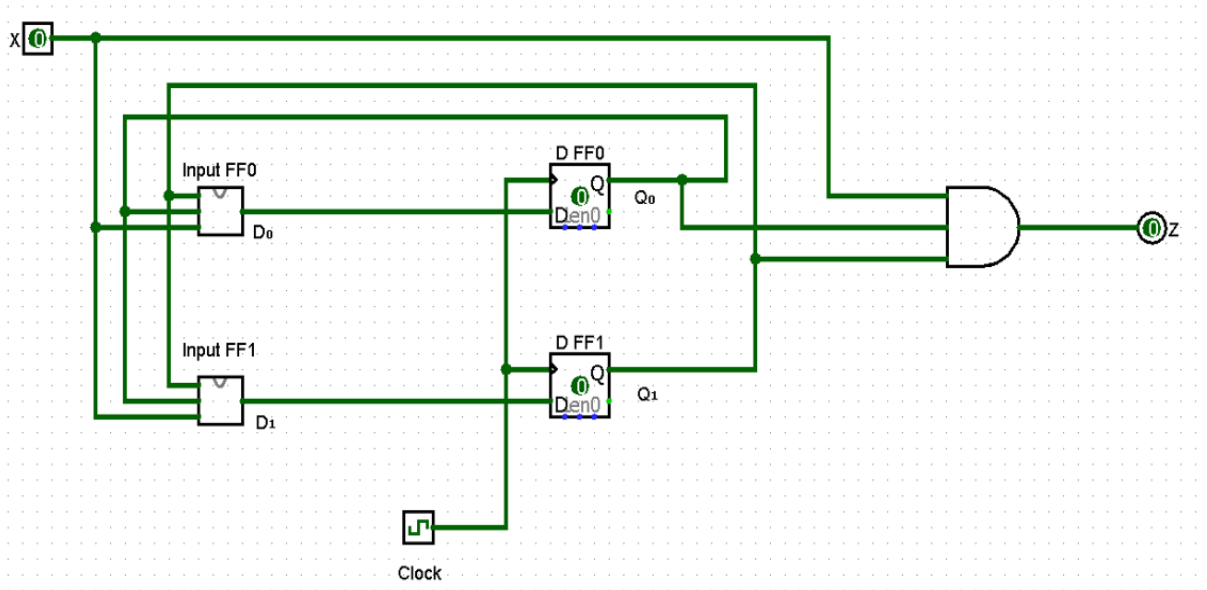
## 1.6.2 Main circuit


The main circuit consists of two D flip-flops.



## 1.7 Circuit simulation


**Input test : 101001**

Step 1 : Set X = 1 [101001]

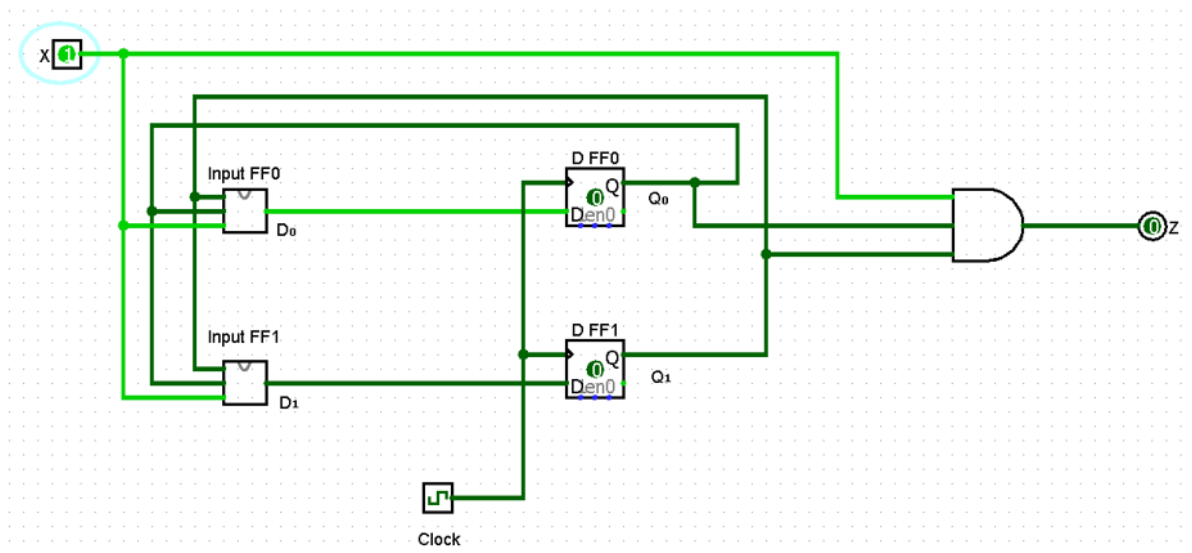


➤  $Z = 0$ . Sequence 1001 is not detected. The sequence 1 has been detected.

Step 2 : Toggle clock

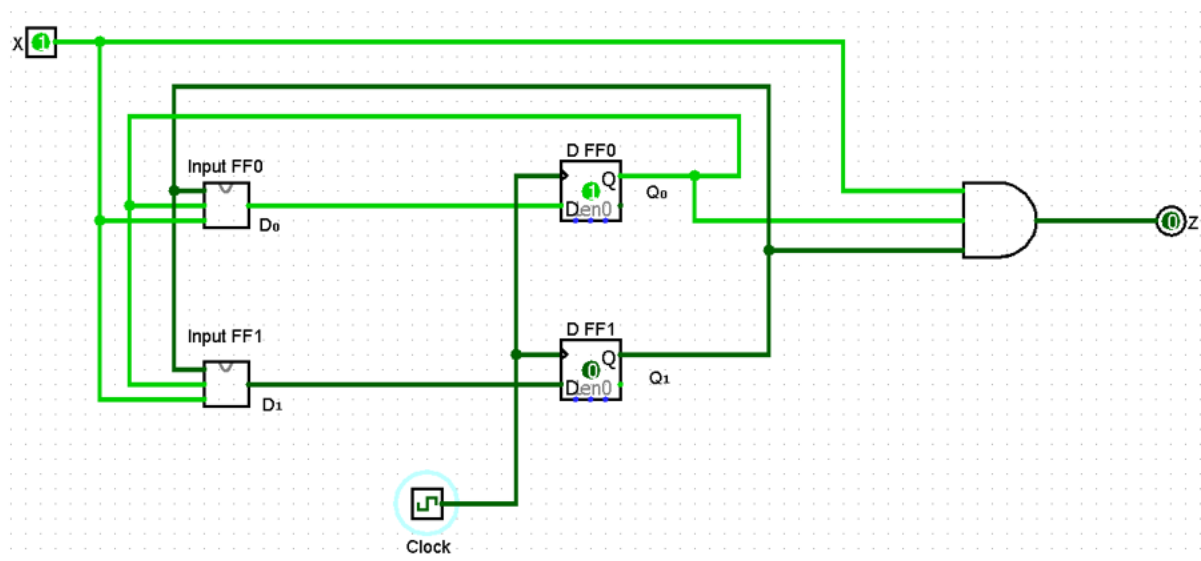

➤ Since  $Q_1 Q_0 = 01$ , circuit is in state B.


Step 3 : Set  $X = 0$  [101001]

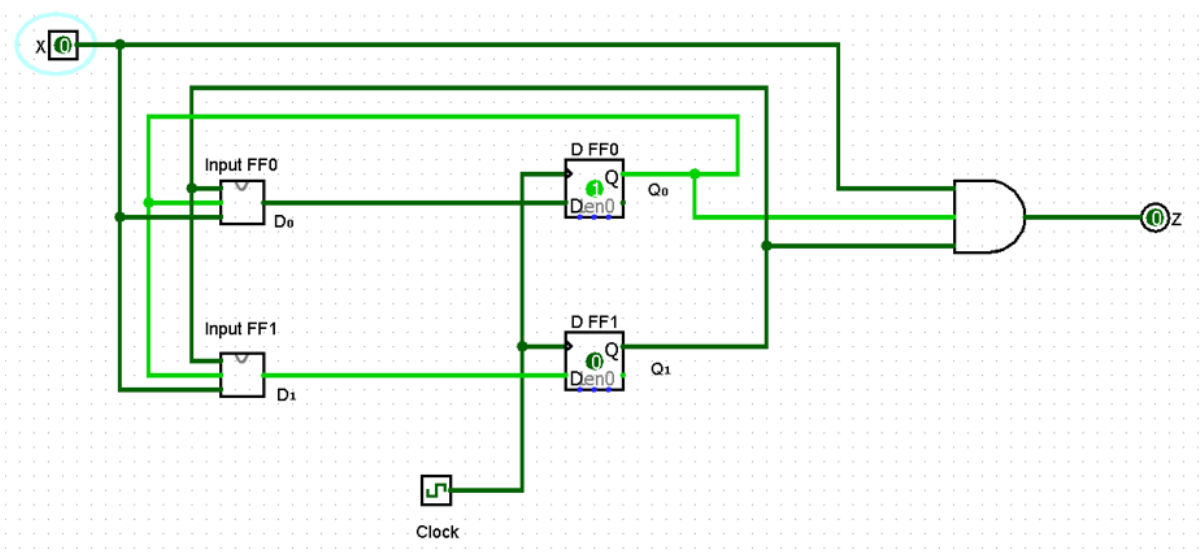

➤  $Z = 0$ . Sequence 1001 is not detected.




Step 4 : Toggle clock

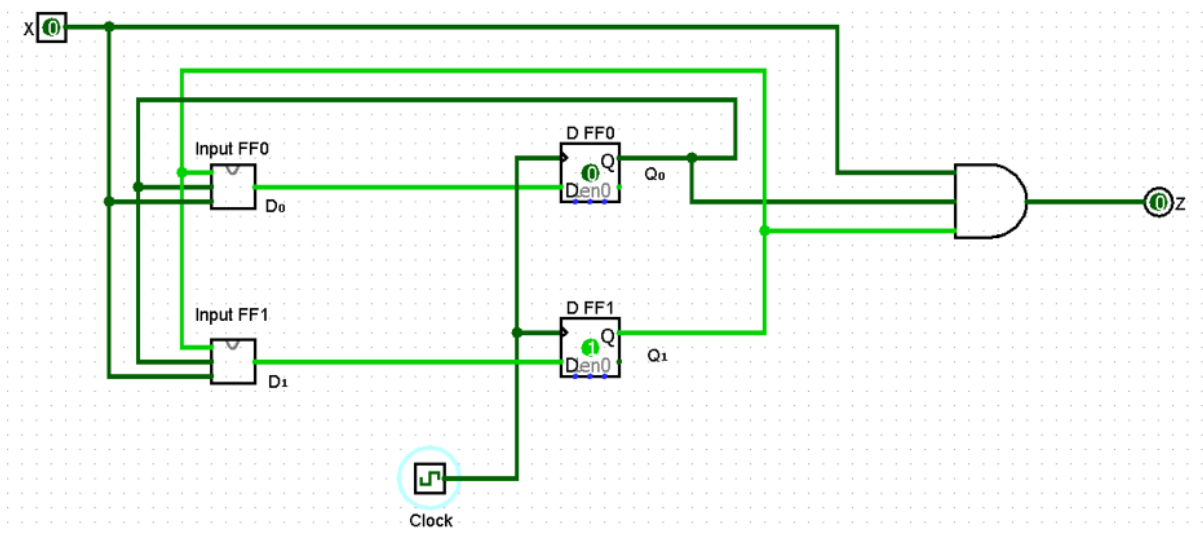


➤ Since  $Q_1 Q_0 = 10$ , circuit moves to state C.

Step 5 : Set  $X = 1$  [101001]

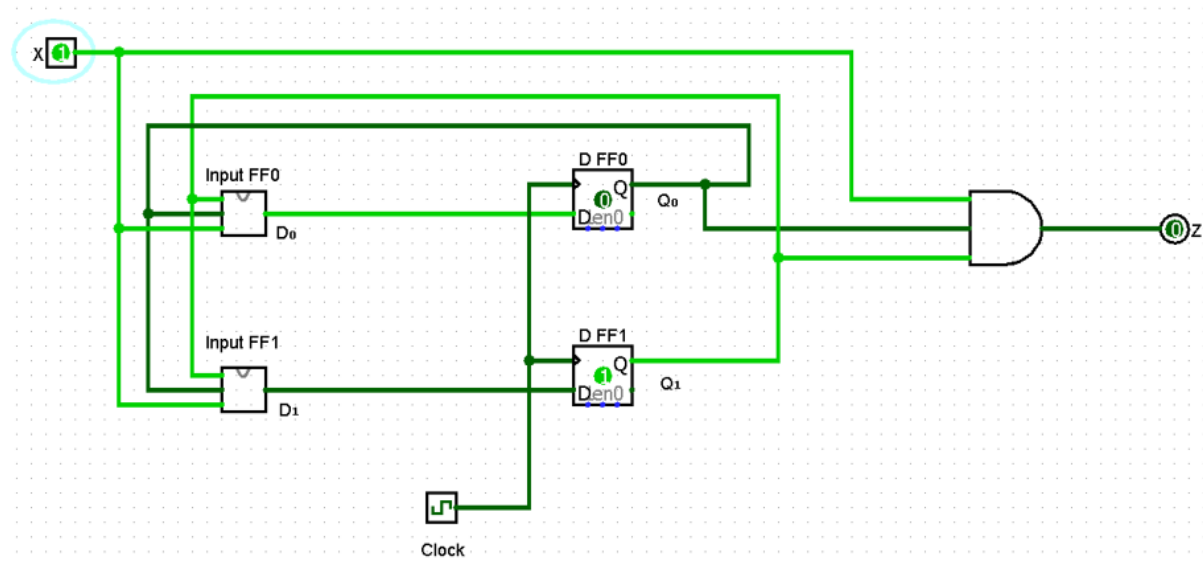


➤  $Z = 0$ . Sequence 1001 is not detected. The sequence 1 has been detected.

Step 6 : Toggle clock

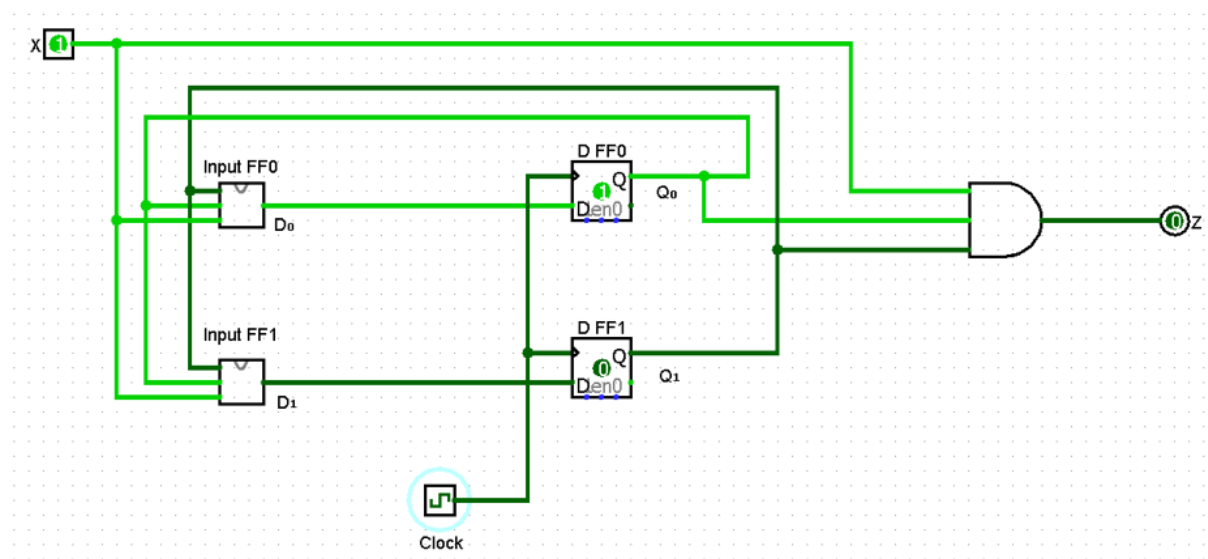


➤ Since  $Q_1 Q_0 = 01$ , circuit moves to state B.

Step 7 : Set  $X = 0$  [101001]

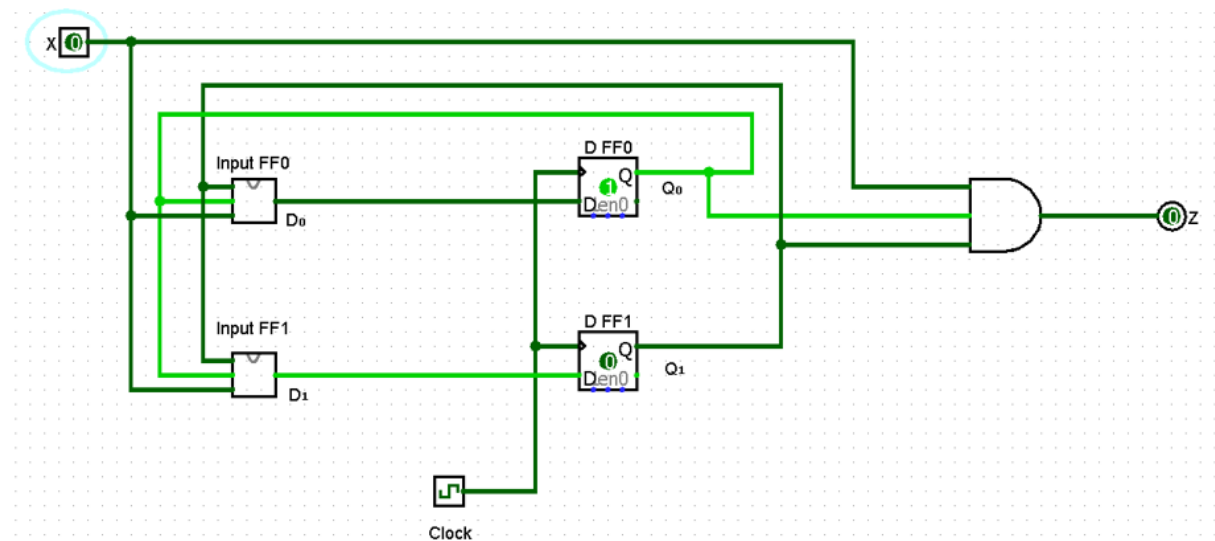


➤  $Z = 0$ . Sequence 1001 is not detected. The sequence 10 has been detected.

Step 8 : Toggle clock

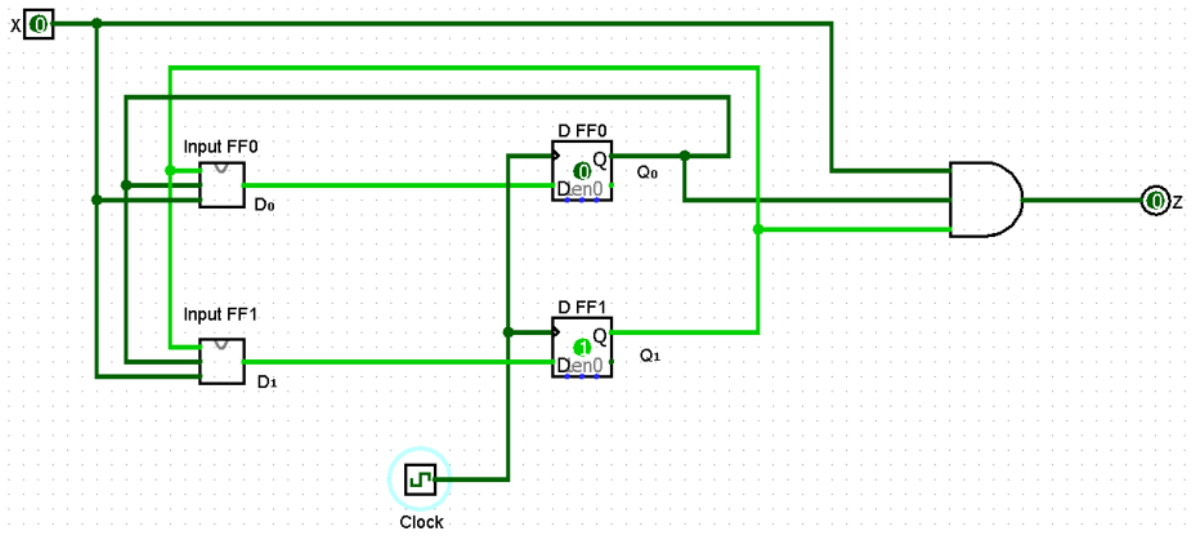


➤ Since  $Q_1 Q_0 = 10$ , circuit moves to state C.

Step 9 : Set  $X = 0$  [101001]

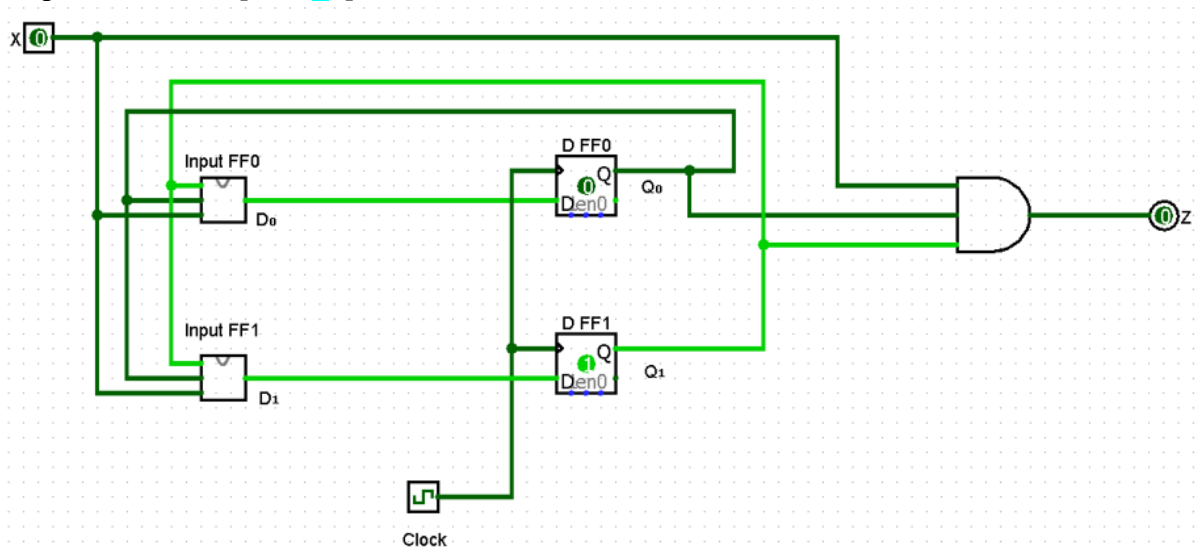


➤  $Z = 0$ . Sequence 1001 is not detected. The sequence 100 has been detected.

Step 10 : Toggle clock

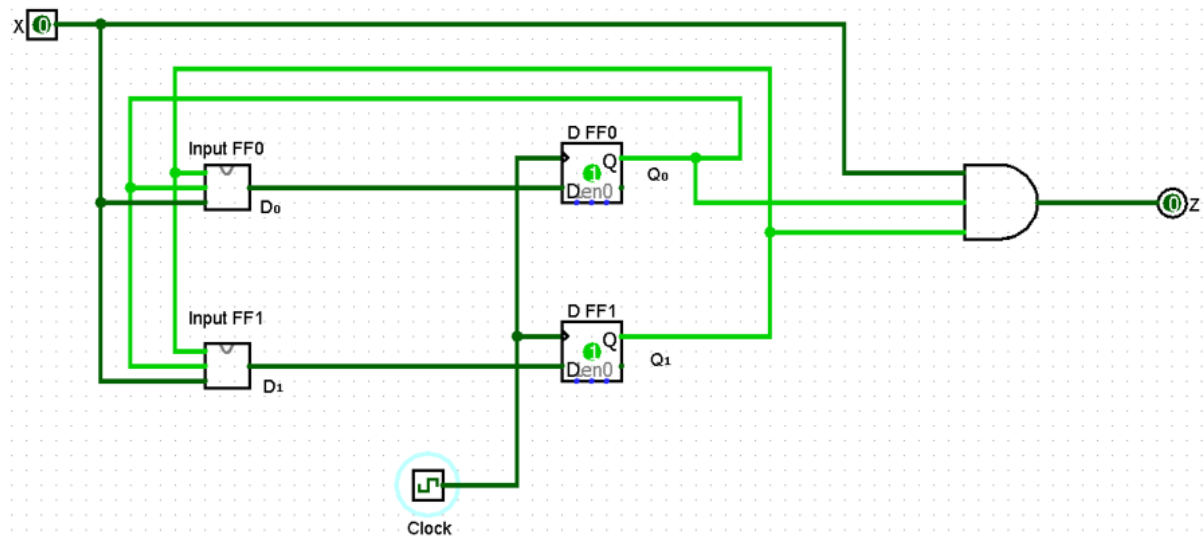


➤ Since  $Q_1 Q_0 = 11$ , circuit moves to state D.

Step 11 : Set  $X = 1$  [101001]

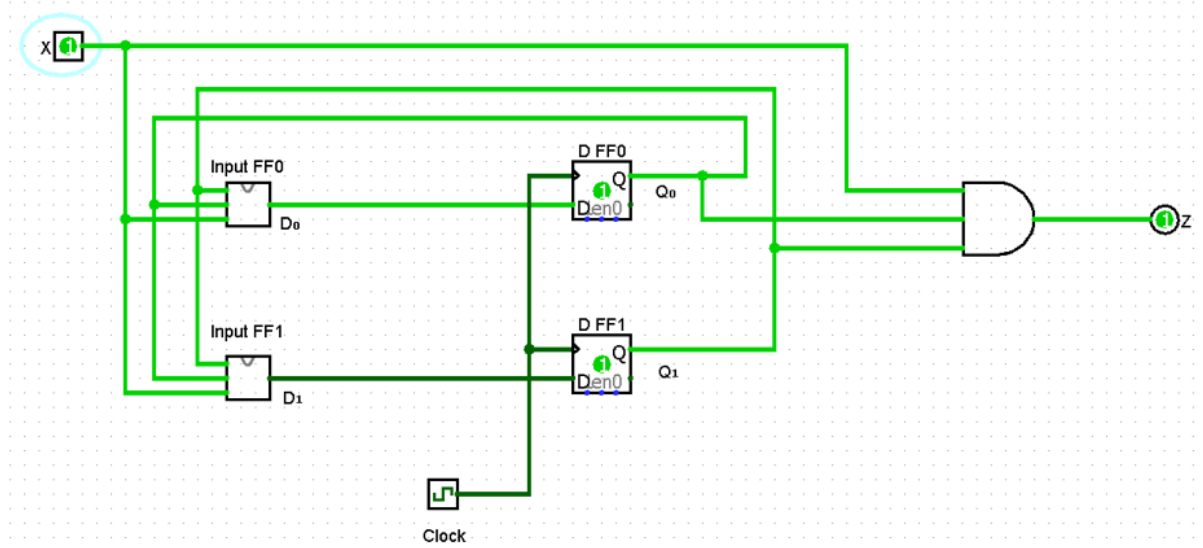

➤  $Z = 1$ . Sequence 1001 has been detected.

Step 12 : Toggle clock

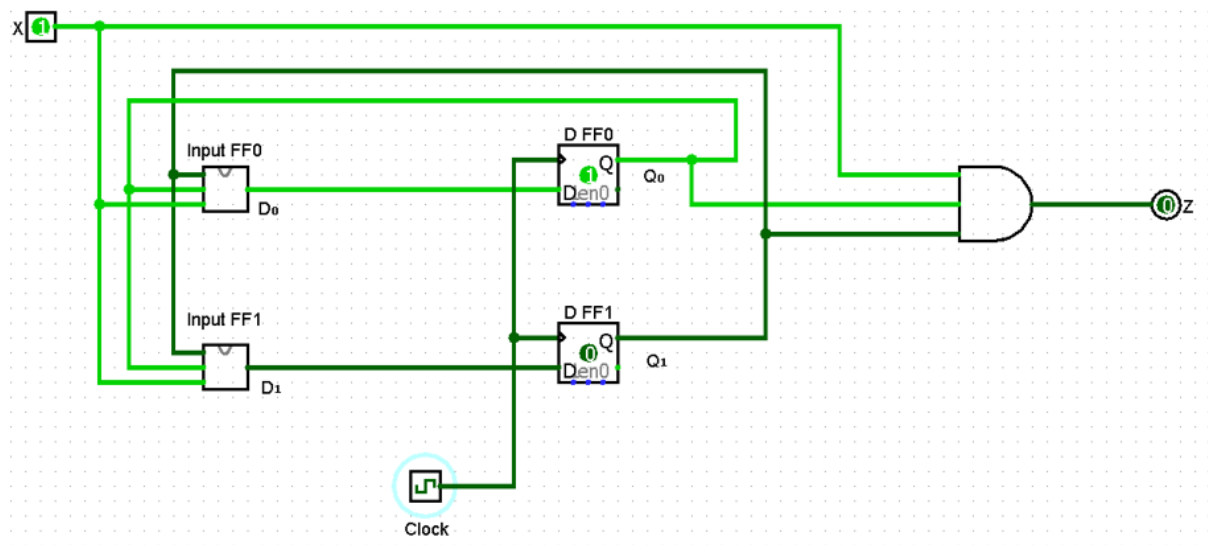


➤ Since  $Q_1 Q_0 = 01$ , circuit moves to state B.

## 2. Vending machine problem

You are to build a FSM (sequential circuit) for a vendor machine which can take only Rs 10 and Rs 5 coins via a coin slot. The vendor machine has internal mechanisms to deliver a can drink AND/OR change. Assuming a can drink costs Rs 20, build the sequential circuit to control the vendor machine.

### 2.1 State transition diagram

State	Meaning	Q <sub>1</sub> Q <sub>0</sub>
S0	No money has been inserted	0 0
S1	Rs 5 has been inserted	0 1
S2	Rs 10 has been inserted	1 0
S3	Rs 15 has been inserted	1 1

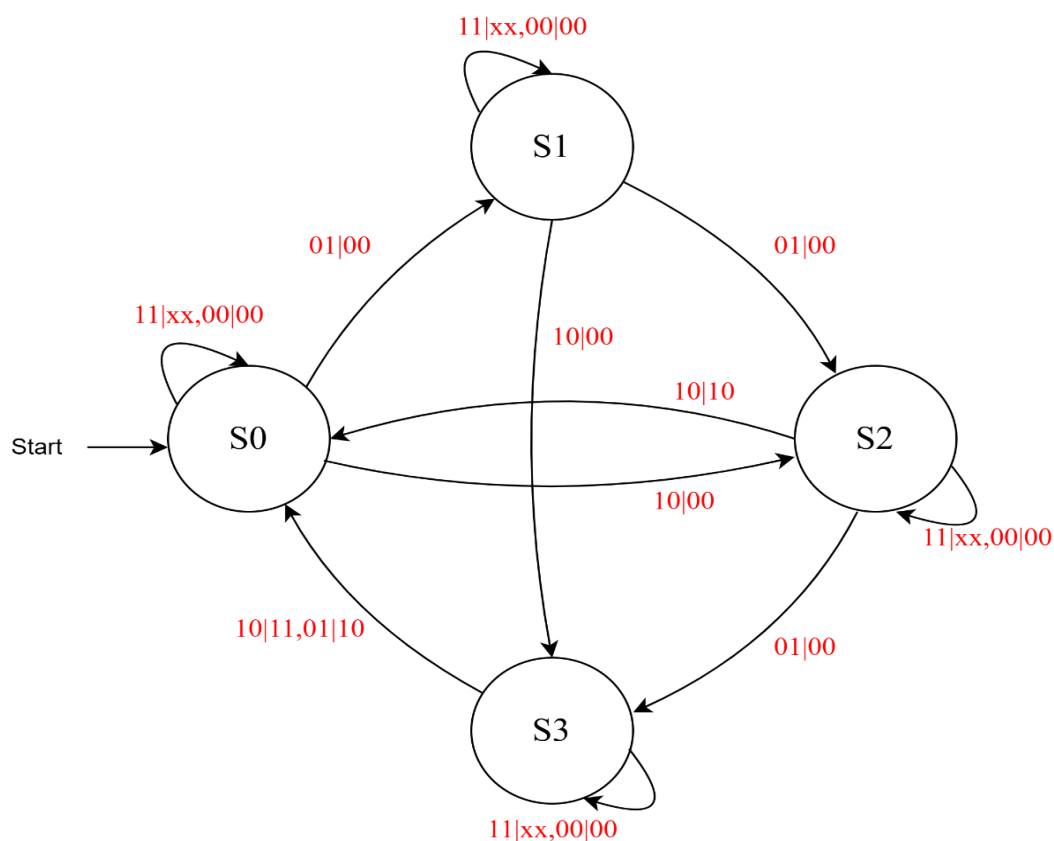

**Notation : TF|DC where T = Rs 5 , F = Rs 10 , D = Drink , C = Change**

## 2.2 State table

Present State	Input		Next State	Output	
	T	F		D	C
S0	0	0	S0	0	0
S0	0	1	S1	0	0
S0	1	0	S2	0	0
S0	1	1	S0	X	X
S1	0	0	S1	0	0
S1	0	1	S2	0	0
S1	1	0	S3	0	0
S1	1	1	S1	X	X
S2	0	0	S2	0	0
S2	0	1	S3	0	0
S2	1	0	S0	1	0
S2	1	1	S2	X	X
S3	0	0	S3	0	0
S3	0	1	S0	1	0
S3	1	0	S0	1	1
S3	1	1	S3	X	X

State	Q <sub>1</sub>	Q <sub>0</sub>
S0	0	0
S1	0	1
S2	1	0
S3	1	1

## 2.3 Assigned binary code to states

Present State	Input		Next State		Output	
	T	F	Q <sub>1</sub>	Q <sub>0</sub>	D	C
S0	0	0	0	0	0	0
S0	0	1	0	1	0	0
S0	1	0	1	0	0	0
S0	1	1	0	0	X	X
S1	0	0	0	1	0	0
S1	0	1	1	0	0	0
S1	1	0	1	1	0	0
S1	1	1	0	1	X	X
S2	0	0	1	0	0	0
S2	0	1	1	1	0	0
S2	1	0	0	0	1	0
S2	1	1	1	0	X	X
S3	0	0	1	1	0	0
S3	0	1	0	0	1	0
S3	1	0	0	0	1	1
S3	1	1	1	1	X	X

## 2.4 Determined flip-flop input values

**D excitation table :**

<b>Q<sub>1</sub></b>	<b>Q<sub>0</sub></b>	<b>D</b>	<b>Operation</b>
0	0	0	Reset
0	1	1	Set
1	0	0	Reset
1	1	1	Set

<b>Present State</b>		<b>Input</b>		<b>Next State</b>		<b>Output</b>		<b>Flip-Flop</b>	
<b>Q<sub>1</sub></b>	<b>Q<sub>0</sub></b>	<b>T</b>	<b>F</b>	<b>Q<sub>1</sub></b>	<b>Q<sub>0</sub></b>	<b>D</b>	<b>C</b>	<b>D<sub>1</sub></b>	<b>D<sub>0</sub></b>
0	0	0	0	0	0	0	0	0	0
0	0	0	1	0	1	0	0	0	1
0	0	1	0	1	0	0	0	1	0
0	0	1	1	0	0	X	X	0	0
0	1	0	0	0	1	0	0	0	1
0	1	0	1	1	0	0	0	1	0
0	1	1	0	1	1	0	0	1	1
0	1	1	1	0	1	X	X	0	1
1	0	0	0	1	0	0	0	1	0
1	0	0	1	1	1	0	0	1	1
1	0	1	0	0	0	1	0	0	0
1	0	1	1	1	0	X	X	1	0
1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	0	1	0	0	0
1	1	1	0	0	0	1	1	0	0
1	1	1	1	1	1	X	X	1	1



## 2.5 Karnaugh maps

For D :

Q <sub>1</sub> Q <sub>0</sub>		00	01	11	10
TF	00	0	0	0	0
	01	0	0	1	0
	11	X	X	X	X
	10	0	0	1	1

$$D = TQ_1 + FQ_1Q_0$$

For C :

Q <sub>1</sub> Q <sub>0</sub>		00	01	11	10
TF	00	0	0	0	0
	01	0	0	0	0
	11	X	X	X	X
	10	0	0	1	0

$$C = TQ_1Q_0$$

For D<sub>1</sub> :

Q <sub>1</sub> Q <sub>0</sub>		00	01	11	10
TF	00	0	0	1	1
	01	0	1	0	1
	11	0	0	1	1
	10	1	1	0	0

$$D_1 = \bar{T}\bar{F}Q_1 + \bar{T}Q_1\bar{Q}_0 + \bar{T}F\bar{Q}_1Q_0 + TFQ_1 + T\bar{F}\bar{Q}_1$$

For D<sub>0</sub> :

Q <sub>1</sub> Q <sub>0</sub>		00	01	11	10
TF	00	0	1	1	0
	01	1	0	0	1
	11	0	1	1	0
	10	0	1	0	0

$$D_0 = \bar{T}\bar{F}Q_0 + \bar{T}F\bar{Q}_0 + TFQ_0 + T\bar{Q}_1Q_0$$

## 2.6 Logic circuits

### 2.6.1 Subcircuits

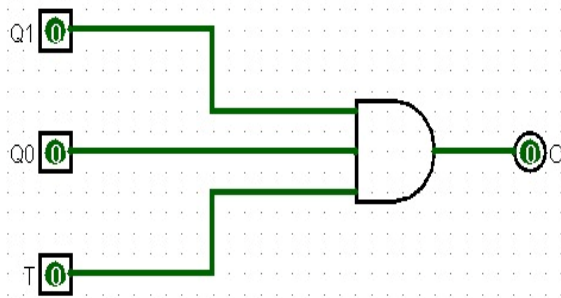


Figure 4 - Output C (Give change)

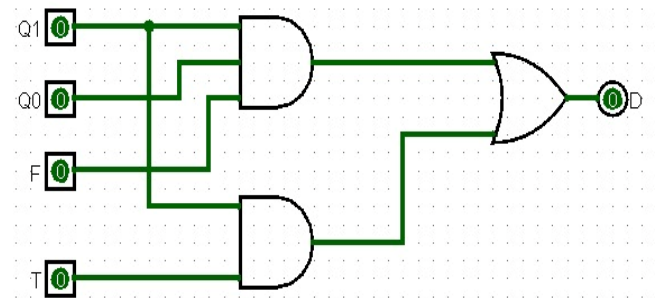


Figure 5 - Output D (Give drink)

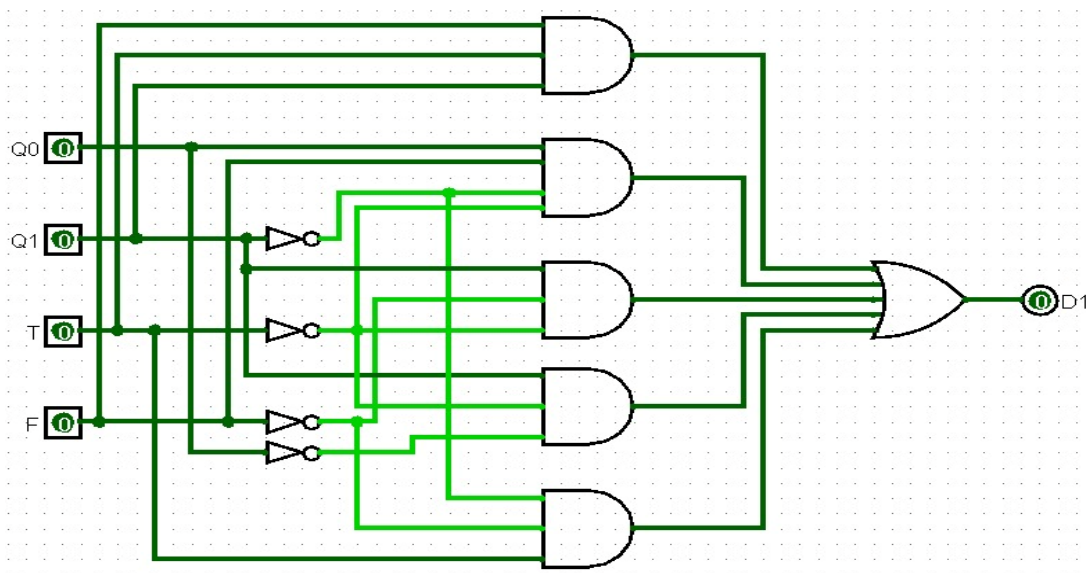


Figure 6 - D Flip-flop 1


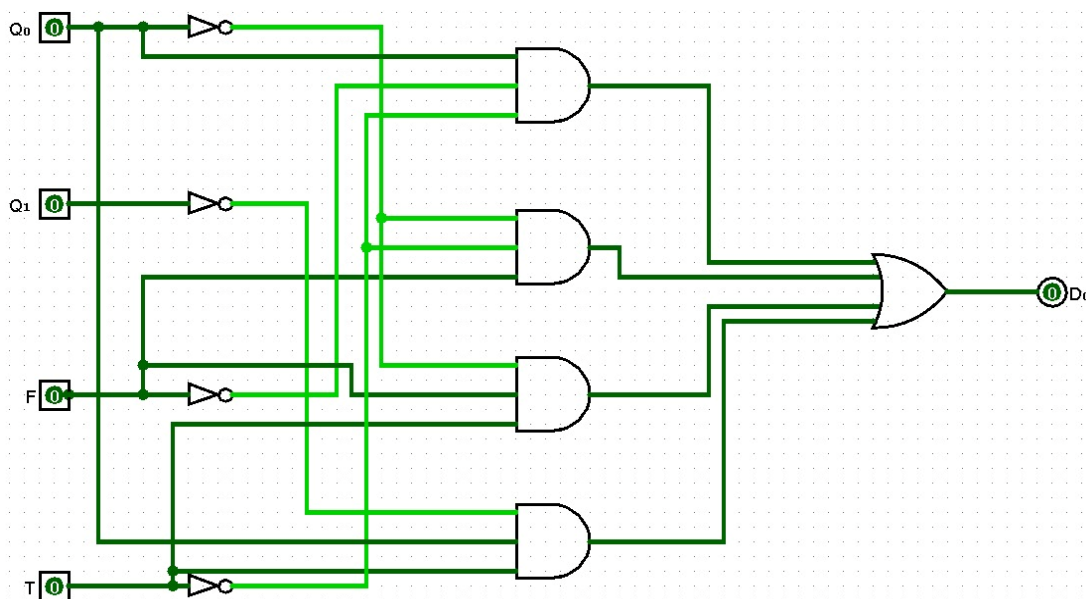


Figure 7 - D Flip-flop 0
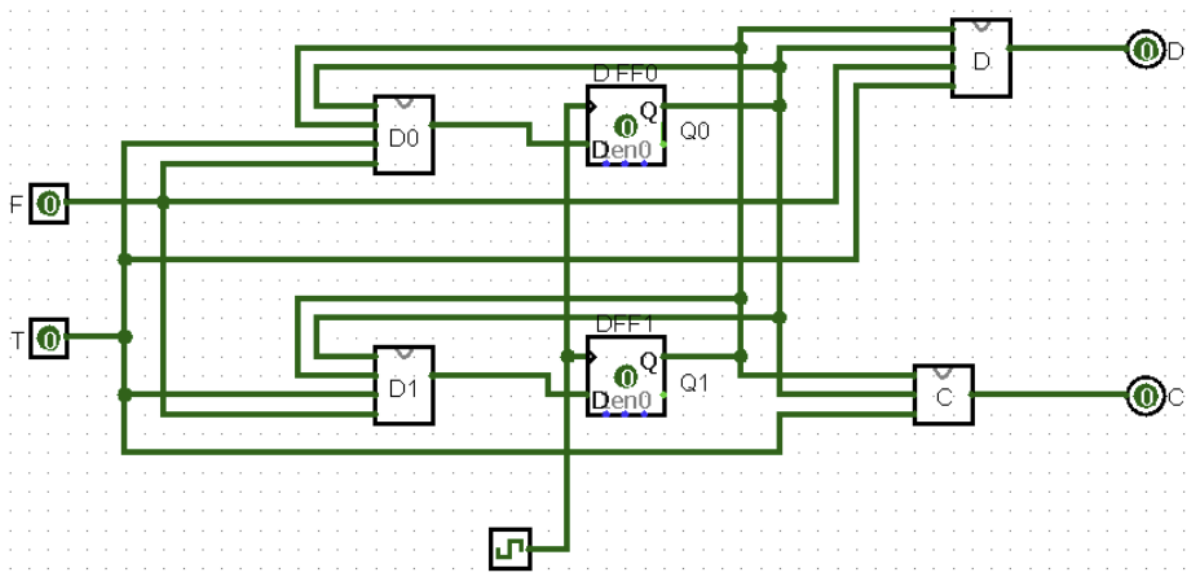
## 2.6.2 Main circuit


The main circuit consists of two D flip-flops.



## 2.7 Circuit simulation


**Input test 1 : 10,5,5**

Step 1 : Set T = 1 [10,5,5]

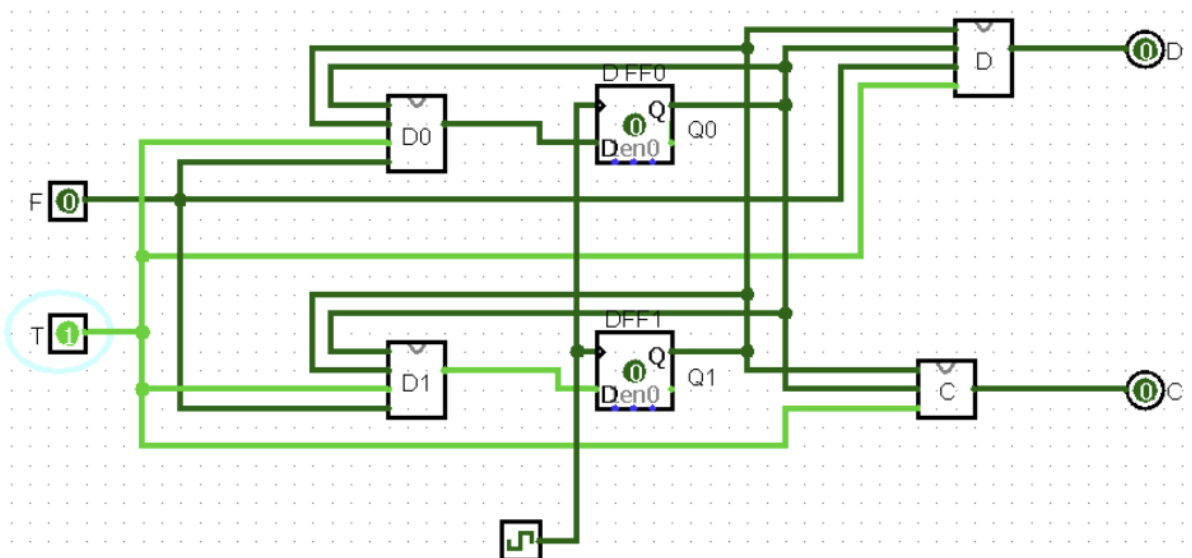


➤ C = 0 , D = 0. Machine takes no action.

Step 2 : Toggle clock then reset T.

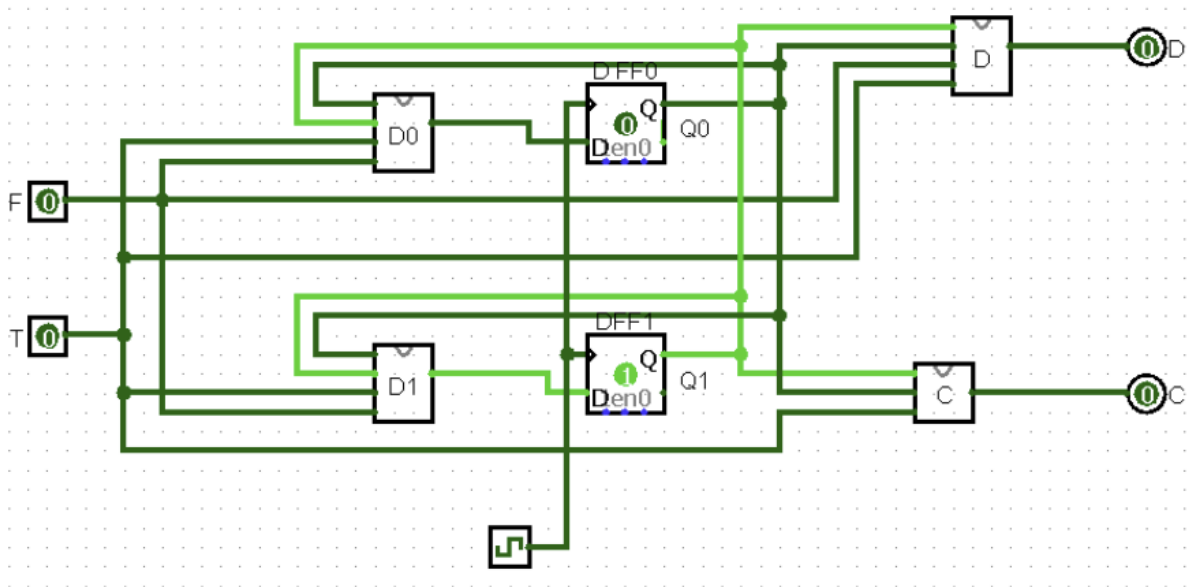


➤ Since  $Q_1Q_0 = 10$ , circuit is in state S2.

Step 3 : Set  $F = 1$  [10,5,5]

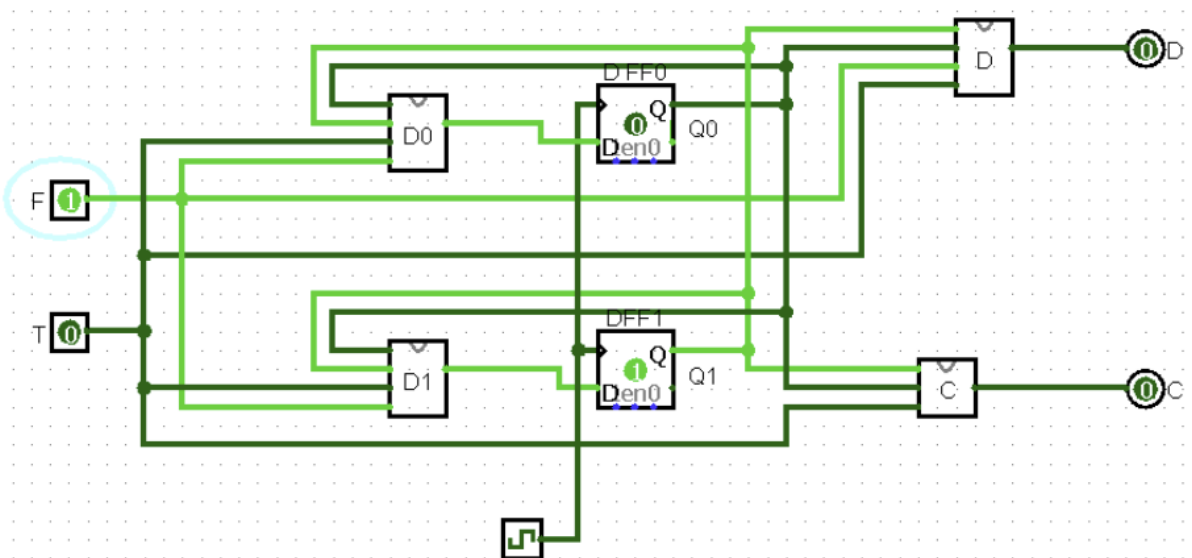


➤  $C = 0$  ,  $D = 0$ . Machine takes no action.

Step 4 : Toggle clock then reset F.

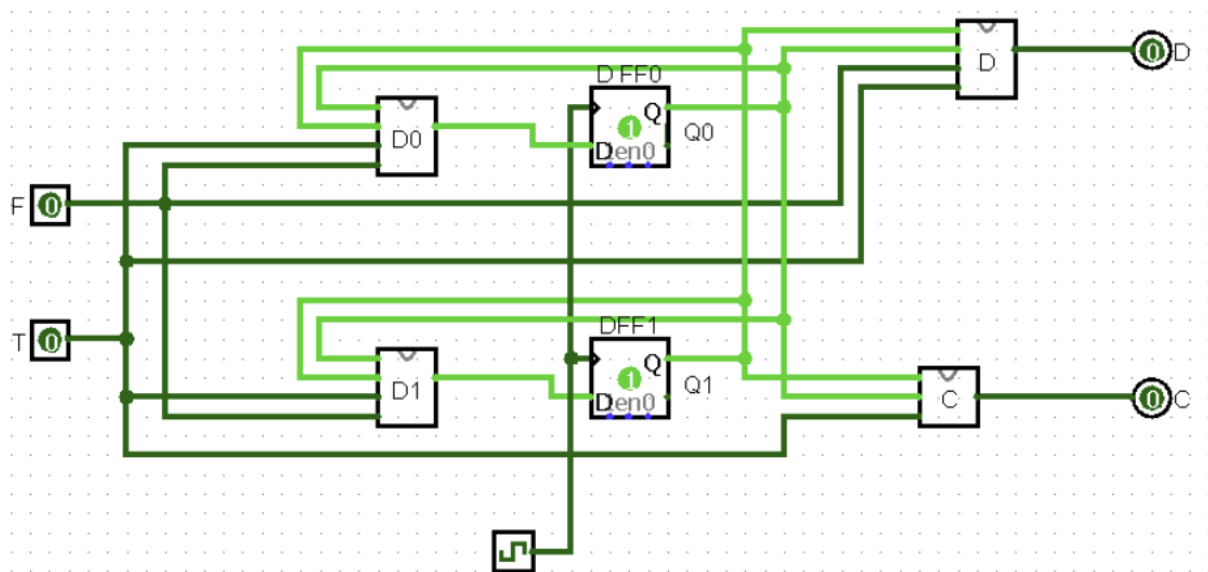


➤ Since  $Q_1Q_0 = 11$ , circuit moves to state S3.

Step 5 : Set  $F = 1$  [10,5,5]

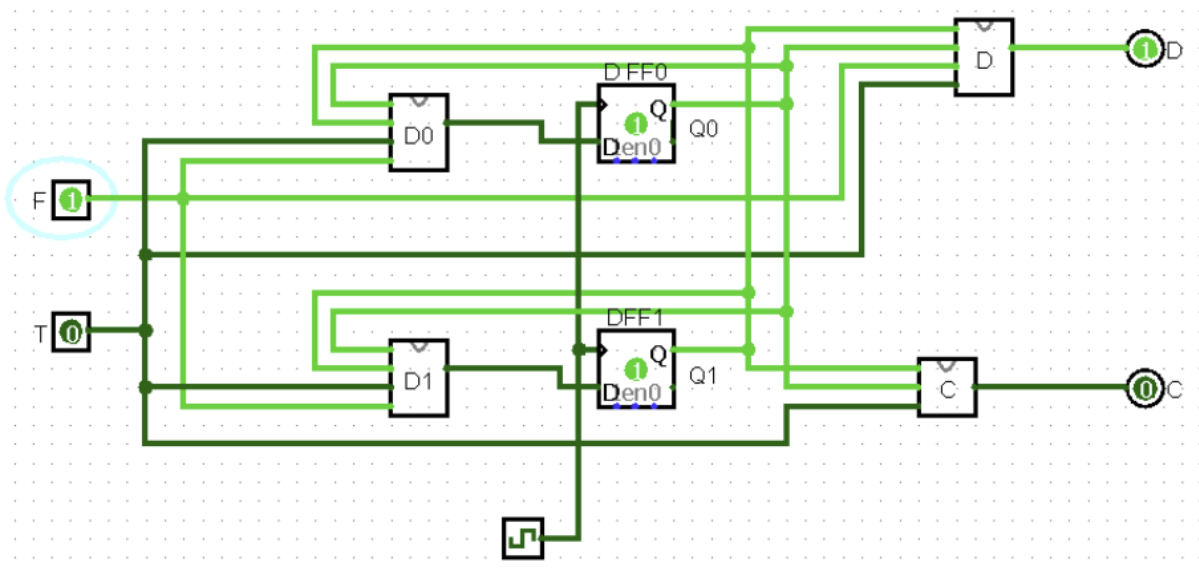

➤  $C = 0$ ,  $D = 1$ . Machine must give drink only.


Step 6 : Toggle clock then reset F.

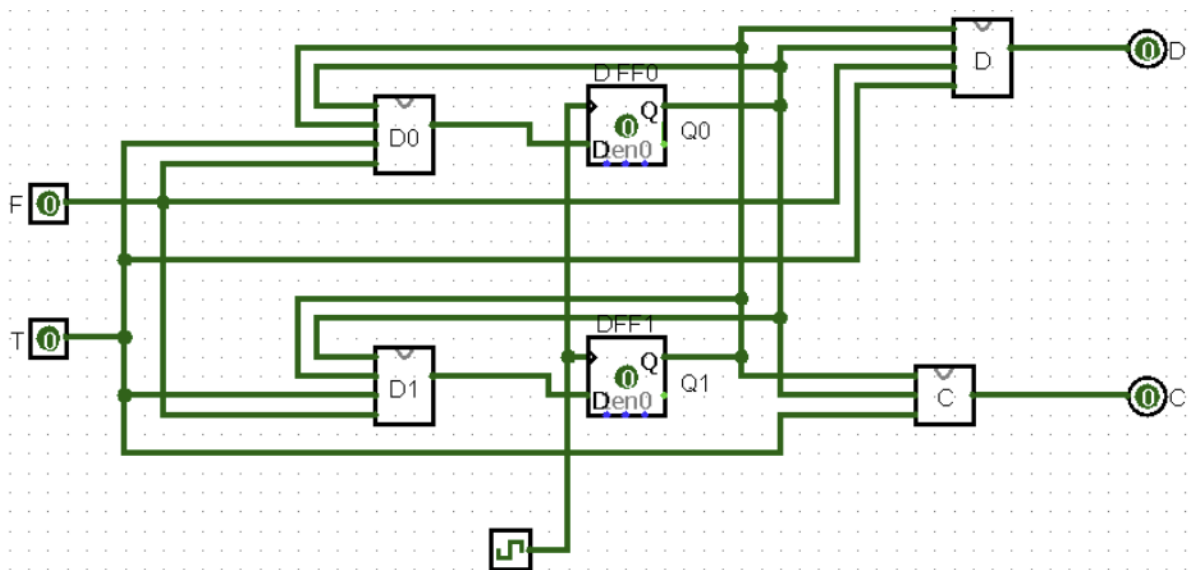

➤ Since  $Q_1Q_0 = 00$ , circuit moves to state S0.


## Input test 2 : 5,5,5,10

Step 1 : Set F = 1 [5,5,5,10]

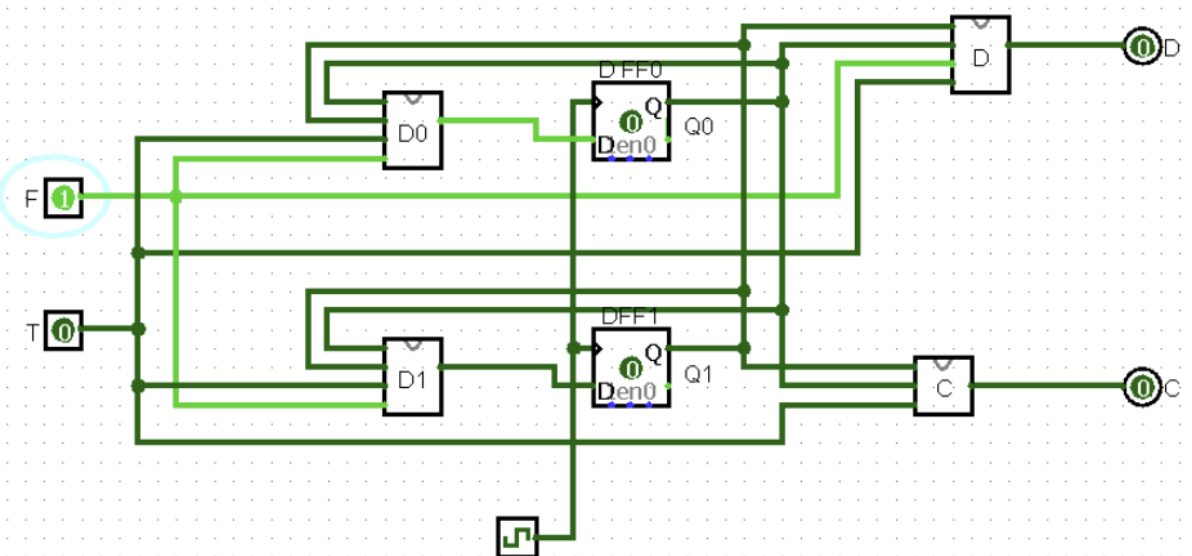


➤  $C = 0$  ,  $D = 0$ . Machine takes no action.

Step 2 : Toggle clock then reset F.

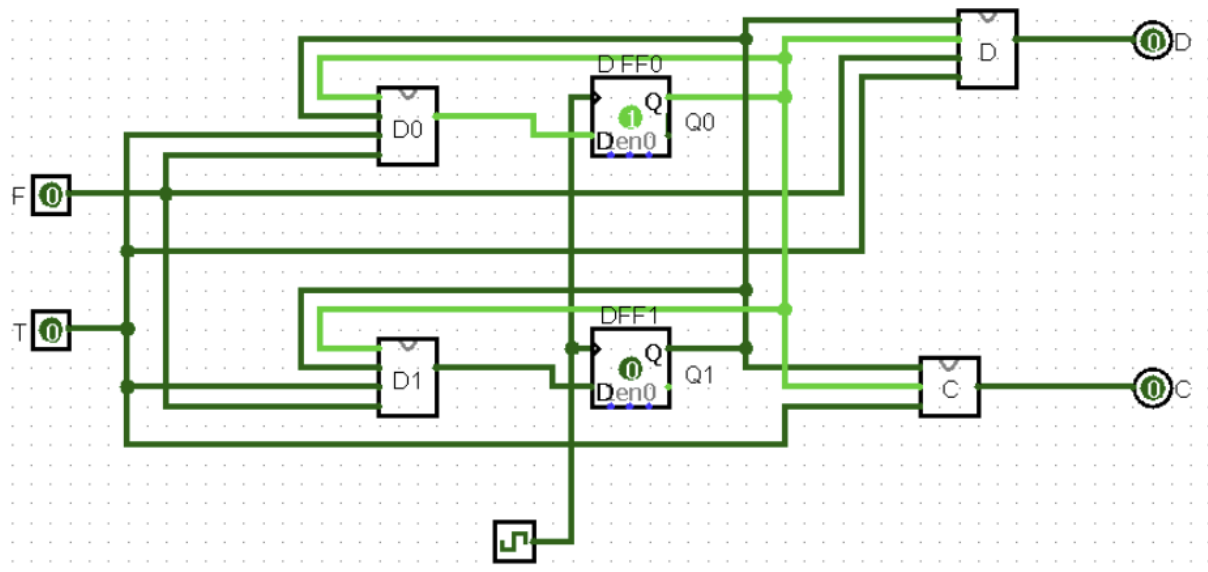


➤ Since  $Q_1Q_0 = 01$ , circuit is in state S1.

Step 3 : Set F = 1 [5,5,5,10]

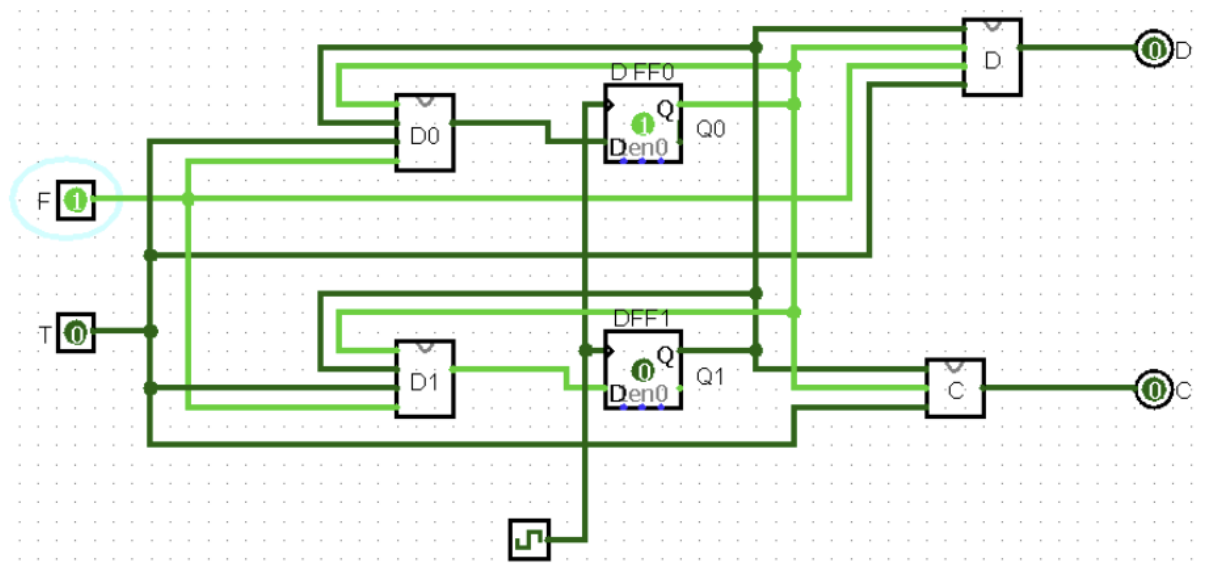


➤  $C = 0$ ,  $D = 0$ . Machine takes no action.

Step 4 : Toggle clock then reset F.

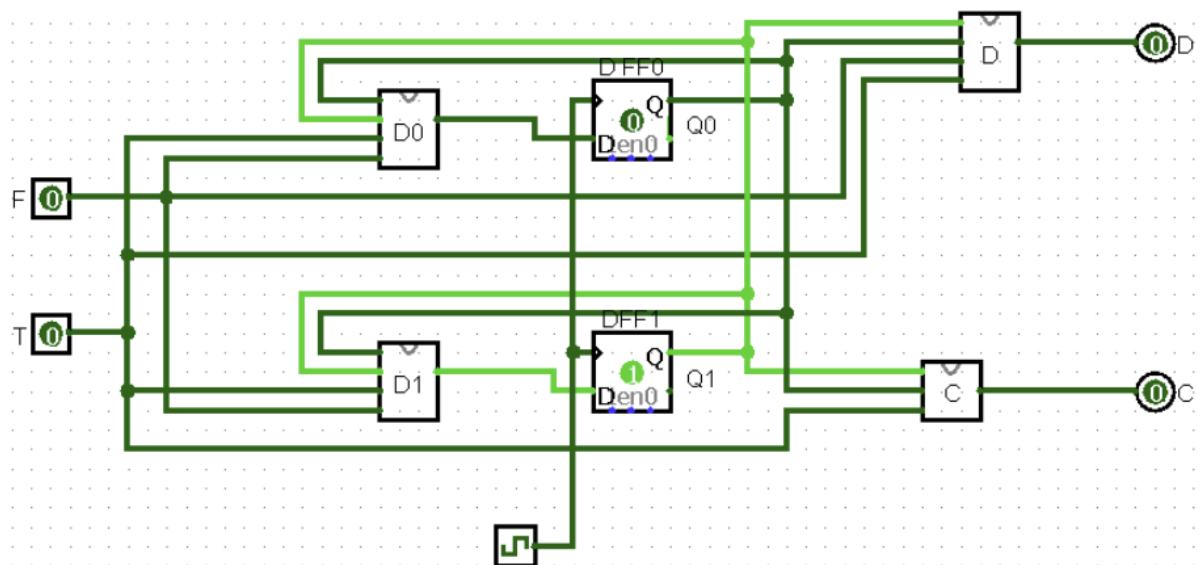

➤ Since  $Q_1Q_0 = 10$ , circuit moves to state S2.


Step 5 : Set F = 1 [5,5,5,10]

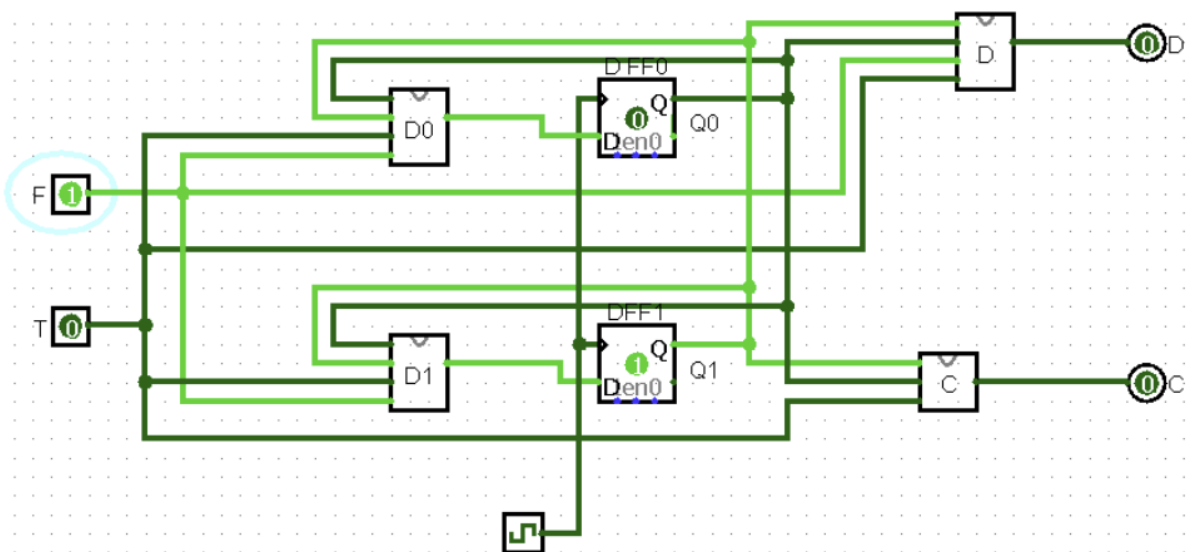

➤  $C = 0$  ,  $D = 0$ . Machine takes no action.




Step 6 : Toggle clock then reset F.

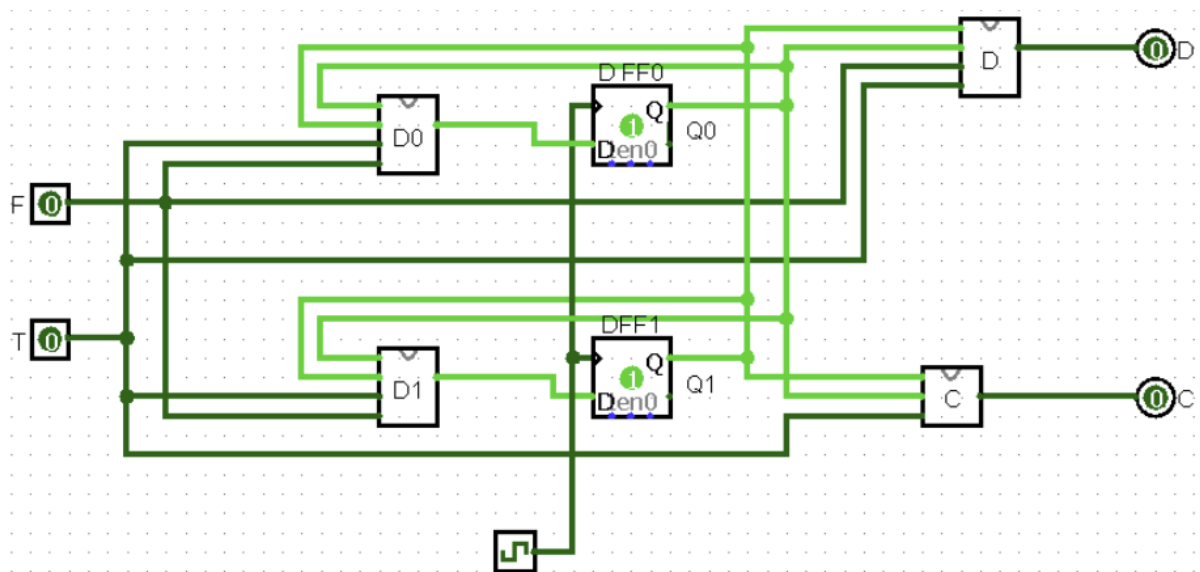


➤ Since  $Q_1Q_0 = 11$ , circuit moves to state S3.

Step 7 : Set  $T = 1$  [5,5,5,10]

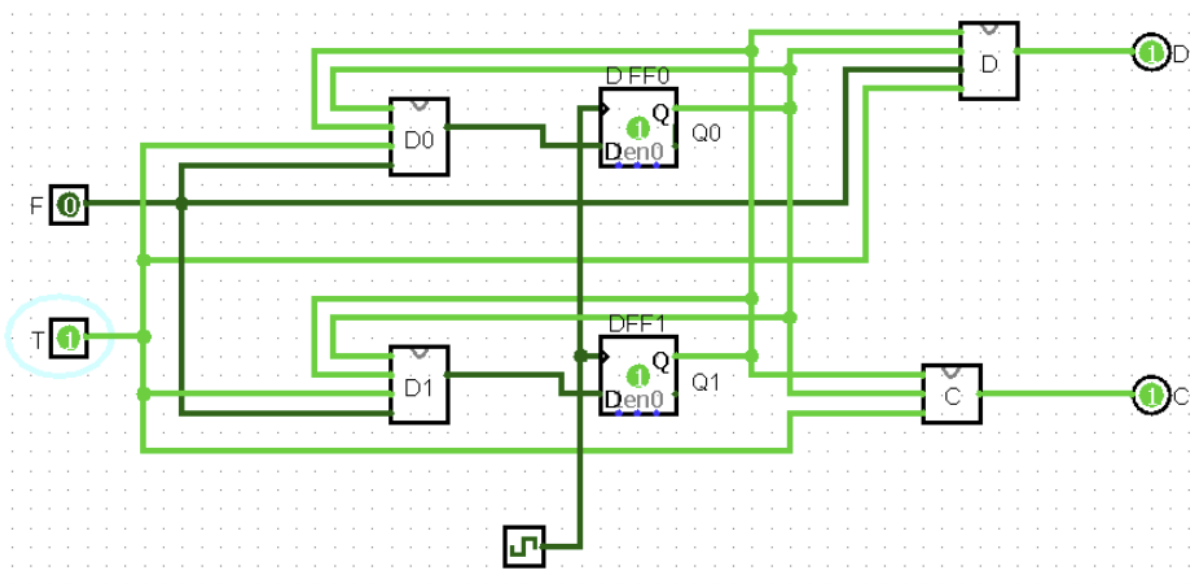

➤  $C = 1$  ,  $D = 1$ . Machine must give drink and change.

Step 8 : Toggle clock then reset T.

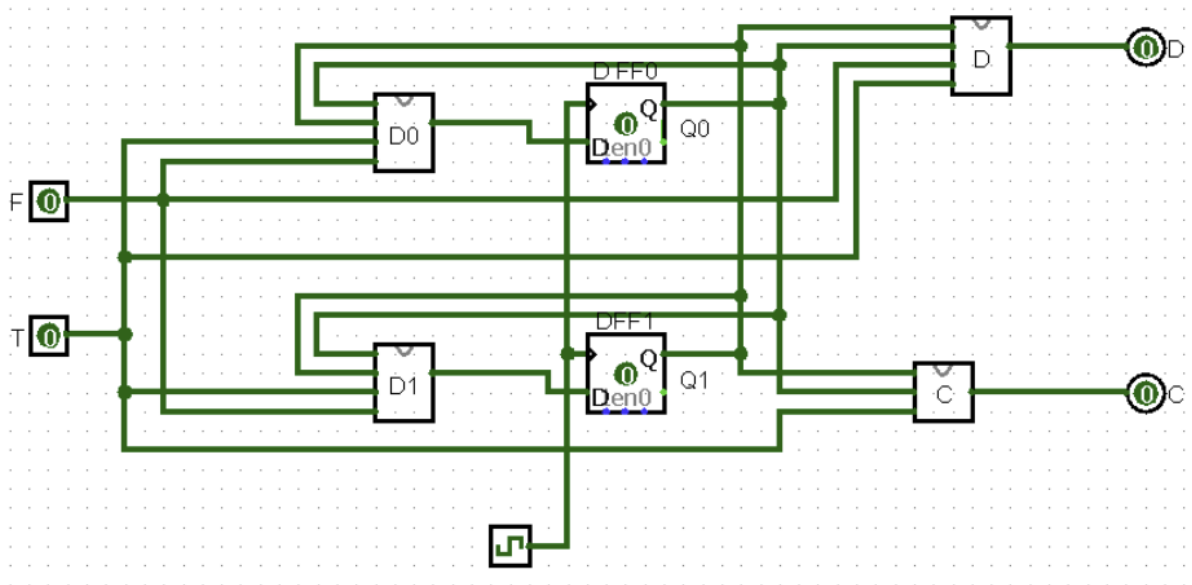

Since  $Q_1Q_0 = 00$ , circuit moves to state S0.